

Kathmandu University
Department of Computer Science and Engineering
Dhulikhel, Kavre



A Mini Project
Report on
“Design of B²RUM Computer”
[Course Code: COMP 315]

Submitted By:

Rajeshwor Niroula (71)
Usta Adhikari (68)
Bikramaditya Prasad Subedi (75)
Milan Dhamala (73)
Bigen Aryal (77)

Submitted To:

Mr. Pankaj Dawadi

Submission Date:

12th July, 2021

Abstract

We have designed 32*20 memory size computer for our CAO project with total of 31 instructions, 11 MRI, 14 RRI and 6 IOI. These instructions are similar to those we have studied under CAO basic computer design but we have also added few extra instructions of our own design. To implement logical and arithmetic operations we have employed 20 stages of 20-bit ALU connecting to 20-bit AC and a single E flipflop. This design also features other registers namely PC, AR, IR, DR, OUTR, INPR and TR along with S, R, IEN, FGI and FGO as flipflops whose functions are discussed below. For 20-bit data interaction among register we have designed 20-bit CBS and several timing and control lines using 4*16 decoders.

Acknowledgement

We would like to show our gratitude to Mr. Pankaj Raj Dawadi, Assistant professor, Kathmandu University for providing us with an opportunity for implementing the course syllabus into a basic computer model. We would also like to thank him heartily for the guidelines that made this design possible.

Table of Contents

| | |
|---|----|
| Abstract..... | 2 |
| Acknowledgement | 3 |
| List of Figures | 5 |
| List of Tables | 6 |
| Acronyms | 7 |
| Chapter 1: Introduction | 8 |
| Chapter 2: Design Consideration | 9 |
| Designing Instructions..... | 10 |
| Instruction Cycle | 13 |
| Interrupt Cycle | 16 |
| Designing Control and Timing Unit: | 17 |
| Chapter 3: Design of Individual Units | 19 |
| Chapter 4: Conclusion | 41 |

List of Figures

| | |
|--|----|
| Figure 1: Structure of Basic Computer | 9 |
| Figure 2: Design of IR | 9 |
| Figure 3: Interrupt Cycle Flowchart..... | 17 |
| Figure 4: Timing and Control Unit | 18 |
| Figure 5: Sequence Counter | 20 |
| Figure 6: Program Counter | 22 |
| Figure 7: Address Register..... | 23 |
| Figure 8: Bit layout in IR | 24 |
| Figure 9: Instruction Register with Decoders | 25 |
| Figure 10: Data Register | 26 |
| Figure 11: Temporary Register | 26 |
| Figure 12: Output Register..... | 27 |
| Figure 13: Input Register | 27 |
| Figure 14: Right Implementation of E flip flop | 30 |
| Figure 15:Start-stop flip flop | 31 |
| Figure 16: FGI Flip flop..... | 31 |
| Figure 17: FGO Flip flop | 31 |
| Figure 18: IEN Flip flop | 32 |
| Figure 19: R Flip flop | 32 |
| Figure 20: Common Bus System | 35 |
| Figure 21: Add and subtract logic..... | 35 |
| Figure 22: Single stage ALU | 38 |
| Figure 23: Accumulator | 40 |
| Figure 24: ALU with AC and E flip flop | 41 |

List of Tables

| | |
|---|----|
| Table 1: List of Register | 10 |
| Table 2: MRI Code | 11 |
| Table 3: RRI Code | 12 |
| Table 4: IOI Code | 12 |
| Table 5: J and K for E flip flop | 29 |
| Table 6: Encoder to selection line..... | 33 |

Acronyms

AR: Address Register
PC: Program Counter
DR: Data Register
TR: Temporary Register
AC: Accumulator
FGI: Input Flag
FGO: Output Flag
MRI: Memory Reference Instruction
CPU: Central Processing Unit
CLR: Clear
RRI: Register Reference Instruction
NOP: No Operation
XOR: Exclusive OR
LDA: Load Accumulator
STA: Store Accumulator
BUN: Branch Unconditionally
CLA: Clear Accumulator
INTR: Increment TR
ION: Interrupt on
IOF: Interrupt off

Chapter 1: Introduction

Our basic computer design has a complex instruction set, it supports basic arithmetic and logic operations such as addition, subtraction, and, or etc. Accumulator is used to store the output of any ALU operation. Data register is used to store data from memory before performing any operations on them. Address register and program counter are both used to specify memory address. Data is transferred between registers using a common address bus. Program counter stores the next instruction to be executed and the computer interfaces with the user using input and output registers. All the instructions are executed by using the signals generated by the control unit consisting of a sequence counter and instruction decoders.

Von Neumann architecture is the design upon which many general purpose computers are based. It consists of three essential different entities: a processing unit, an I/O unit and a storage unit. The units are connected over a common bus. In Von Neumann data and instruction are both stored as binary digits in primary storage. The instructions are fetched from memory one at a time sequentially as controlled by a program counter. The processor decodes and executes an instruction, before cycling around to fetch the next instruction. This cycle continues until no more instructions are available.

A processor based on von Neumann architecture has five special registers which it uses for processing:

- the program counter (PC) holds the memory address of the next instruction to be fetched from primary storage
- the memory address register (MAR) holds the address of the current instruction that is to be fetched from memory, or the address in memory to which data is to be transferred
- the memory data register (MDR) holds the contents found at the address held in the MAR, or data which is to be transferred to primary storage
- the current instruction register (CIR) holds the instruction that is currently being decoded and executed
- the accumulator (ACC) is a special purpose register and is used by the arithmetic logic unit (ALU) to hold the data being processed and the results of calculations

Our basic computer design is based upon the principal of Von Neumann Architecture.

Chapter 2: Design Consideration

For our computer, we have chosen a memory of 32k *20 size.

32k refers to the number of address or slots or words and 20 represents the size of each word.

$$32k = 2^5 * 2^{10} = 2^{15}$$

To represent all this addresses we need 15 bits of data, hence our IR has 15 bits for addresses.

Since, Memory is loaded into IR we need 20 bit IR for 20-word size with 15 bits occupied for address. It leaves us with 5 bits remaining in IR which we used for op-code and addressing mode. Since, our computer has only have 2 types of addressing, direct and indirect, we have used only 1 bit for mode and remaining 4 bits for op-code.

We used total of 8 registers of which AR and PC has 15 bits size because they only store address. INPR and OUTR are of 10 bits because that's our input character and output character size as for all other register they are of 20 bits size.

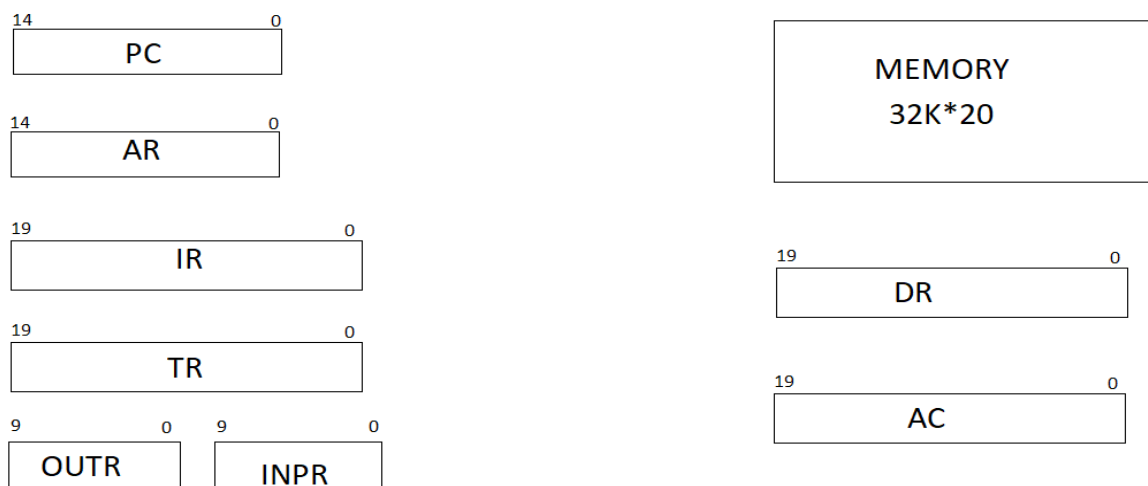


Figure 1: Structure of Basic Computer

- $2^5 = 32$ unique possible instructions
- $32K = 2^5 * 2^{10} = 2^{15} = 32768$ memory locations

 


Figure 2: Design of IR

| Registers | Bits |
|----------------------------------|------|
| DR (Data Register) | 20 |
| AR (Address Register) | 15 |
| AC (Accumulator) | 20 |
| IR (Instruction Register) | 20 |
| PC (Program Counter) | 15 |
| TR (Temporary Register) | 20 |
| INPR (Input Character Register) | 10 |
| OUTR (Output Character Register) | 10 |

Table 1: List of Register

Designing Instructions

We have three types of instruction as described below:

- **MRI (Memory Reference Instruction):** Like the name says these instructions deal with operations over memory stored data, for our computer we have designed 11 MRI instructions. These instructions can be identified by checking op-code bits. Anything but $(1111)_2$ for op-code is going to be an MRI instruction. These instructions are decoded from 18th, 17th, 16th and 15th bits of IR by a 4*16 decoder giving us (D_0-D_{15}) of which (D_0-D_{10}) represents MRI as tabulated below:

| Decoder | Operation | I | Op-code | | | | I | Op-code | | | |
|-----------------|-----------|---|---------|---|---|---|---|---------|---|---|---|
| D ₀ | AND | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| D ₁ | ADD | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| D ₂ | LDA | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| D ₃ | STA | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| D ₄ | BUN | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| D ₅ | BSA | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 1 |
| D ₆ | ISZ | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| D ₇ | OR | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| D ₈ | SUB | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| D ₉ | XOR | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| D ₁₀ | NAND | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 |

Table 2:MRI Code

- **RRI (Register Reference Instruction):** These instructions deal with operations over register stored data and doesn't involve memory. We have designed 14 RRI instructions. This instruction can be identified by checking op-code bits. In T₃ timing for I=0 if op-code= (1111)₂ its RRI since (1111)₂ activates decoder D₁₅, we can write above convention as:

$$I'.D_{15}.T_3=r$$

where r is common of all RRI instructions as for identifying individual instructions, we decode the address bits to give decoder output (B₀-B₁₃) which will represent 14 RRI as tabulated below:

| INSTRUCTION | CODE | DECODER |
|-------------|-------|-----------------|
| CLA | 78000 | B ₀ |
| CLE | 78001 | B ₁ |
| CMA | 78002 | B ₂ |
| CME | 78003 | B ₃ |
| CIR | 78004 | B ₄ |
| CIL | 78005 | B ₅ |
| INC | 78006 | B ₆ |
| SPA | 78007 | B ₇ |
| SNA | 78008 | B ₈ |
| SZA | 78009 | B ₉ |
| SZE | 78010 | B ₁₀ |
| HLT | 78011 | B ₁₁ |
| TIRA | 78012 | B ₁₂ |
| TDRA | 78013 | B ₁₃ |

Table 3: RRI Code

- **IOI(Input Output Instruction):** It deals with the input and output operations and can be identified in T₃ timing for I=1 if op-code = (1111)₂ its IOI. IOI uses same decoder as RRI and uses (B₀-B₅) to represent IOI instructions.

$$I.D_{15}.T_3=p$$

These instructions are tabulated below:

| Instruction | Code | Decoder |
|-------------|-------|----------------|
| INP | F8000 | B ₀ |
| OUT | F8001 | B ₁ |
| SKI | F8002 | B ₂ |
| SKO | F8003 | B ₃ |
| ION | F8004 | B ₄ |
| IOF | F8005 | B ₅ |

Table 4: IOI Code

Instruction Cycle

Instruction cycle comprises of fetch, decode and execute cycle. The first two stage, fetch and decode are similar to all instructions, only execution will differ.

$$R'T_0 : AR \leftarrow PC$$

For timing T_0 address pointed by program counter is transferred to AR.

$$R'T_1 : IR \leftarrow M[AR], PC \leftarrow PC+1$$

For timing T_1 , memory of address in AR is stored in Instruction Register (IR) and program counter is incremented by 1 so that it can point to next instruction in the memory. This step is also known as fetch cycle.

$$R'T_2 : I \leftarrow IR(19), D_0-D_{15} \leftarrow IR(18,17,16,15), AR \leftarrow IR(14-0)$$

For timing T_2 , 19th bit of IR is used as I bit, 18-15th bit selects a decoder output from (D_0-D_{15}).

As for remaining bits, they are stored in AR as address bits. This is also known as a decode cycle.

Once the decode is complete, process enters into timing T_3 where there are four possible outcomes.

$$1. D_{15}.I.T_3 : NOP$$

For any decoder output except D_{15} , if the addressing mode is direct i.e $I'(0)$, no operation will occur and computer transitions to T_4 cycle.

$$2. D_{15}.I.T_3 : AR \leftarrow M[AR]$$

For any decoder output except D_{15} , if the addressing mode is indirect i.e $I(1)$ memory stored in the address of AR is stored back into AR and the computer transitions to T_4 cycle.

$$3. D_{15}.I'.T_3 : r$$

For D_{15} decoder output if the I bit equals to 0 it refers to RRI instructions.

$$4. D_{15}.I.T_3 : p$$

For D_{15} decoder output if the I bit equals 1 it refers to IOI instruction.

After T_3 timing signal is complete, computer transitions to T_4 timing signal from where execution of instructions begins.

MRI

AND:

$$D_0.T_4 : DR \leftarrow M[AR]$$

$$D_0.T_5 : AC \leftarrow AC \text{ AND } DR, SC \leftarrow 0$$

ADD to AC:

$D_1T_4 : DR \leftarrow M[AR]$

$D_1T_5 : AC \leftarrow AC + DR, E \leftarrow C_{out}, SC \leftarrow 0$

LDA:

$D_2T_4 : DR \leftarrow M[AR]$

$D_2T_5 : AC \leftarrow DR, SC \leftarrow 0$

STA Store AC:

$D_3T_4 : M[AR] \leftarrow AC, SC \leftarrow 0$

BUN:

$D_4T_4 : PC \leftarrow AR, SC \leftarrow 0$

BSA:

$D_5T_4 : M[AR] \leftarrow PC, AR \leftarrow AR + 1$

$D_5T_5 : PC \leftarrow AR, SC \leftarrow 0$

ISZ:

$D_6T_4 : DR \leftarrow M[AR]$

$D_6T_5 : DR \leftarrow DR + 1$

$D_6T_6 : M[AR] \leftarrow DR, \text{ if } (DR=0) \text{ then } (PC \leftarrow PC + 1), SC \leftarrow 0$

OR:

$D_7T_4 : DR \leftarrow M[AR]$

$D_7T_5 : AC \leftarrow AC \vee DR, SC \leftarrow 0$

SUB:

$D_8T_4 : DR \leftarrow M[AR]$

$D_8T_5 : AC \leftarrow AC - DR, E \leftarrow C_{out}, SC \leftarrow 0$

XOR:

$D_9T_4 : DR \leftarrow M[AR]$

$D_9T_5 : AC \leftarrow AC \oplus DR, SC \leftarrow 0$

NAND:

$D_{10}T_4 : DR \leftarrow M[AR]$

$D_{10}T_5 : AC \leftarrow AC \text{ NAND } DR, SC \leftarrow 0$

Indirect Addressing:

$D_{15}IT_3 : AR \leftarrow M[AR]$

RRI:

$D_{10}I'T_3 : r \quad r:SC \leftarrow 0$

CLA : Clear AC

$rB_0 : AC \leftarrow 0$
 CLE : Clear E
 $rB_1 : E \leftarrow 0$
 CMA : Complement AC
 $rB_2 : AC \leftarrow AC'$
 CME : Complement E
 $rB_3 : E \leftarrow E'$
 CIR : Circulate Right
 $rB_4 : AC \leftarrow shr(AC), AC(19) \leftarrow E, E \leftarrow AC(0)$
 CIL : Circulate Left
 $rB_5 : AC \leftarrow shl(AC), AC(0) \leftarrow E, E \leftarrow AC(19)$
 INC : Increment AC
 $rB_6 : AC \leftarrow AC + 1$
 SPA : Skip if Positive
 $rB_7 : \text{If } (AC(19)=0), \text{ then } PC \leftarrow PC + 1$
 SNA : Skip if Negative
 $rB_8 : \text{If } (AC(19)=1), \text{ then } PC \leftarrow PC + 1$
 SZA : Skip if Zero AC
 $rB_9 : \text{If } AC=0 \text{ then, } PC \leftarrow PC + 1$
 SZE : Skip if Zero E
 $rB_{10} : \text{If } (E=0), \text{ then } PC \leftarrow PC + 1$
 HLT : Halt
 $rB_{11} : S \leftarrow 0$ (S is start/stop flip flop)
 TIRA : Transfer IR to ACC
 $rB_{12} : AC \leftarrow IR$
 TDRA : Transfer DR complement to AC
 $rB_{13} : AC \leftarrow DR'$

IOI:

$D_{15..I.T_3} : p$

$p:SC \leftarrow 0$

INP: Input Character.

$pB_0: AC(0-9) \leftarrow INPR, FGI \leftarrow 0$

OUT: Output Character

$pB_1: OUTF \leftarrow AC(0-9), FGO \leftarrow 0$

SKI: Skip on Input flag.

pB₂: If (FGI=1) then PC \leftarrow PC +1

SKO: Skip on Output flag

pB₃: If (FGO=1) then PC \leftarrow PC+1

ION: Interrupt Enable On

pB₄: IEN \leftarrow 1

IOF: Interrupt Enable Off

pB₅: IEN \leftarrow 0

Interrupt Cycle

Interrupt is a disturbance caused by I/O for inputting data or outputting data. Since CPU is much faster than I/O devices there can be a speed mis-matching, to solve this we use flags to synchronize timing. The system keeps constantly checking for flag bits, R stored in a flip-flop. The IEN flip-flop can be set and cleared with two instructions. For as long as IEN is set to 0, the system cannot be interrupted. Once the IEN is set to 1 the system checks for either FGO or FGI flags. If any of the flags is set to 1 then the flag R is set to 1 and the interrupt cycle begins.

Interrupt can happen with any clock transition except when timing signals T₀, T₁ and T₂ are active.

IEN (FGI+FGO) . T₀' . T₁' . T₂' : R \leftarrow 1

RT₀ : AR \leftarrow 0, TR \leftarrow PC

RT₁ : M[AR] \leftarrow TR, PC \leftarrow 0

RT₂ : PC \leftarrow PC + 1, IEN \leftarrow 0, R \leftarrow 0, SC \leftarrow 0

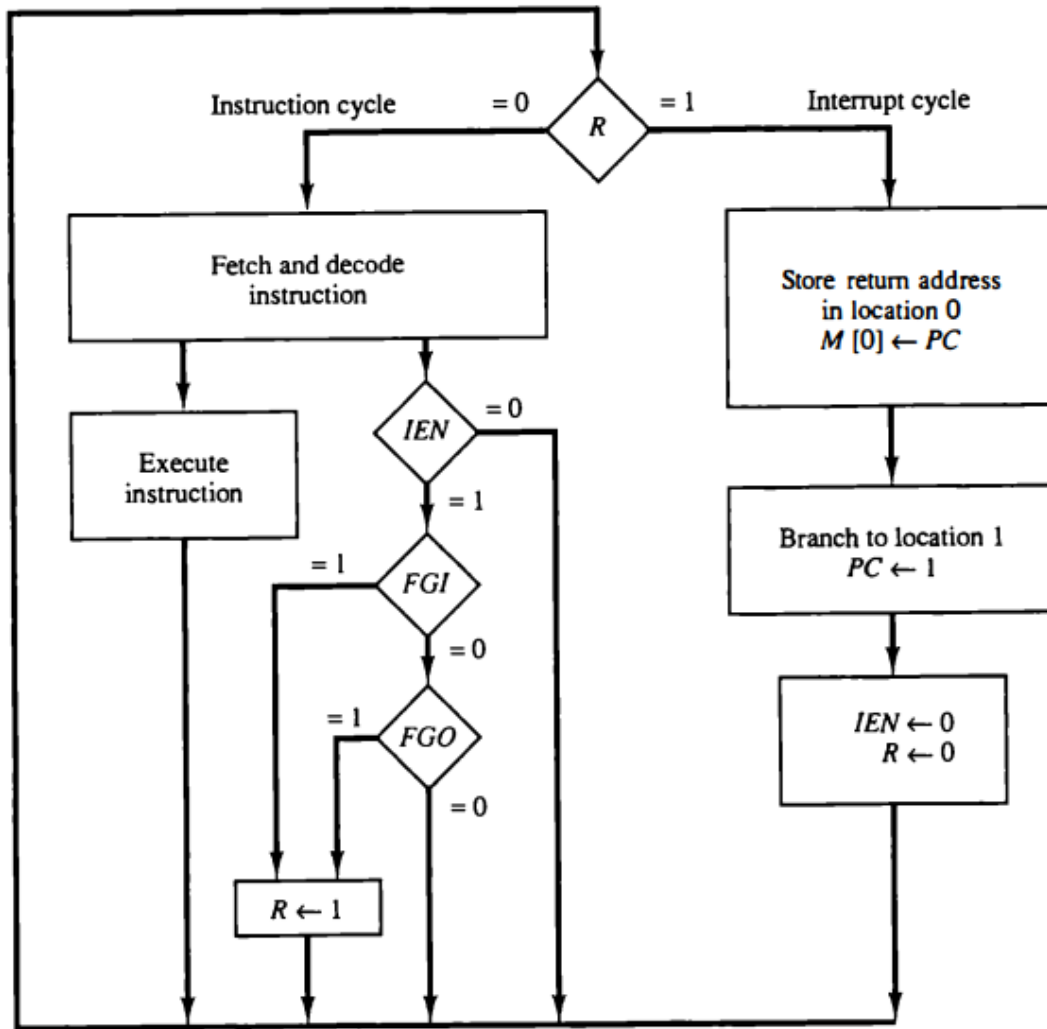


Figure 3: Interrupt Cycle Flowchart

Designing Control and Timing Unit:

Control unit comprises of IR, sequence counter and decoder. 19th bit of IR is used as I bit, 18th-15th bit is decoded to D₀ - D₁₅ and addresses bit will be decoded to B₀ - B₁₃ all of which will be used for controlling registers and flip-flops throughout the computer.

As for timing signals a 4-bit sequence counter is connected to a decoder to give T₀-T₁₅ timing signal. SC is always incremented for every clock except when CLR is set to 1 through instruction cycles or if the timer reaches T₁₅.

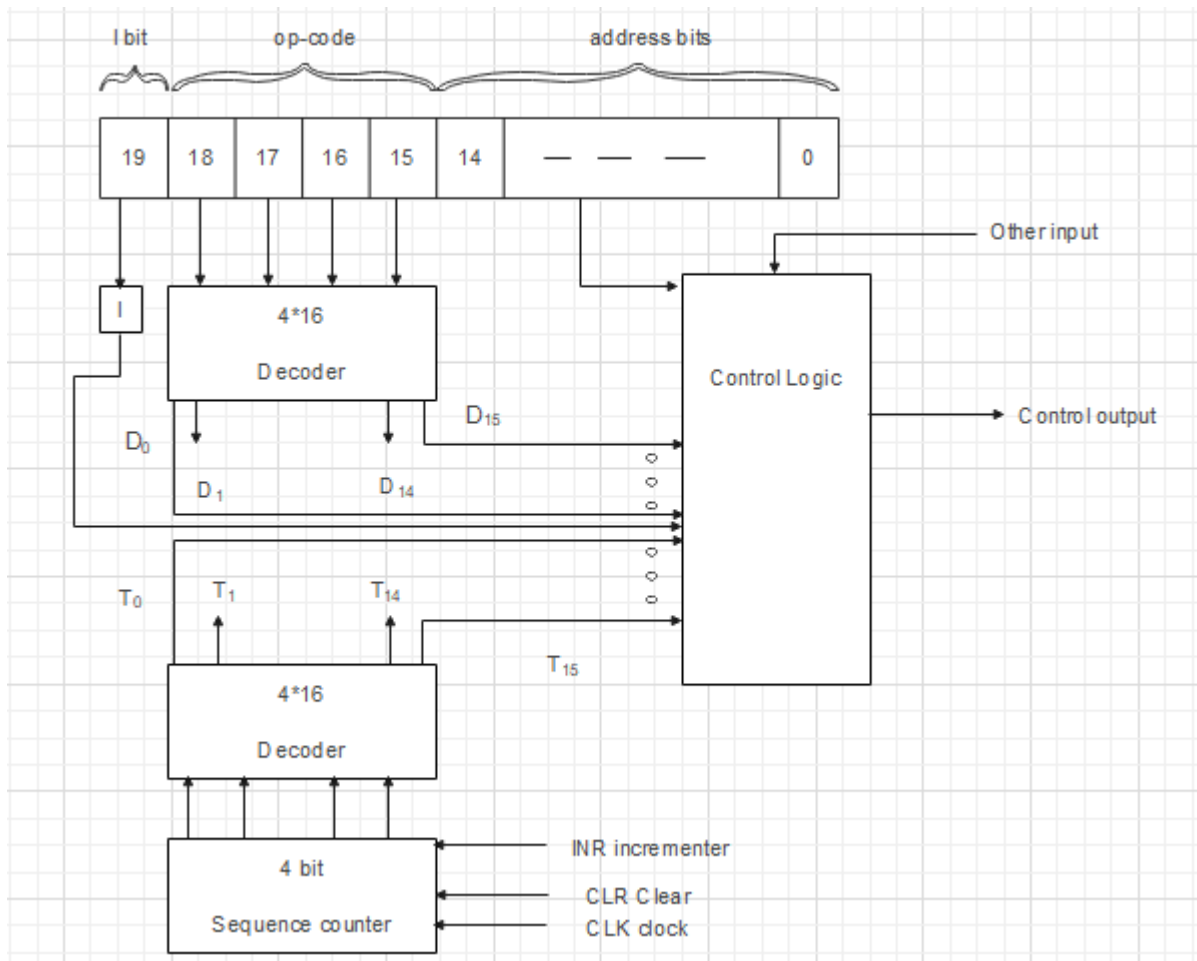


Figure 4: Timing and Control Unit

Chapter 3: Design of Individual Units

SC (Sequence Counter): Much about sequence counter has already been discussed in control and timing unit.

The logic for CLR (Clear) for SC can be obtained by OR-ing all of below conditions:

r:SC \leftarrow 0

D₀T₅ : AC \leftarrow AC AND DR, SC \leftarrow 0

D₁T₅ : AC \leftarrow AC+DR, E \leftarrow C_{out}, SC \leftarrow 0

D₂T₅ : AC \leftarrow DR, SC \leftarrow 0

D₃T₄ : M [AR] \leftarrow AC, SC \leftarrow 0

D₄T₄ : PC \leftarrow AR, SC \leftarrow 0

D₅T₅ : PC \leftarrow AR, SC \leftarrow 0

D₆T₆ : M [AR] \leftarrow DR, if (DR=0) then (PC \leftarrow PC+1), SC \leftarrow 0

D₇T₅ : AC \leftarrow AC v DR, SC \leftarrow 0

D₈T₅ : AC \leftarrow AC - DR, E_S \leftarrow C_{out}, SC \leftarrow 0

D₉T₅ : AC \leftarrow AC \oplus DR, SC \leftarrow 0

D₁₀T₅ : AC \leftarrow AC NAND D R, SC \leftarrow 0

p:SC \leftarrow 0

INR is set to be complement of CLR so that if CLR is not active then SC is constantly incrementing.

 


Figure 5: Sequence Counter

Program Counter (PC) : Program Counter register is used to point to the memory address to be loaded into IR. It is constantly incremented to processing list of instructions.

Logic for PC can be obtained by OR-ing below conditions:

LD:

D₄.T₄ : PC←AR, SC←0

D₅.T₅ : PC←AR, SC←0

CLR:

RT₁ : M[AR] ← TR, PC←0

INR:

R'T₁ : IR←M [AR], PC ← PC+1

pB₂: If (FGI=1) then PC ← PC +1

pB₃: If (FGO=1) then PC ← PC+1

rB₇ : If (AC(19)=0), then PC←PC+1

rB₈ : If (AC(19)=1), then PC←PC+1

rB₉ : If AC=0 then, PC←PC+1

rB₁₀ : If (E=0), then PC←PC+1

RT₂ : PC← PC + 1, IEN ← 0, R←0, SC←0

D₆T₆ : M [AR]←DR, if (DR=0) then (PC←PC+1), SC←0

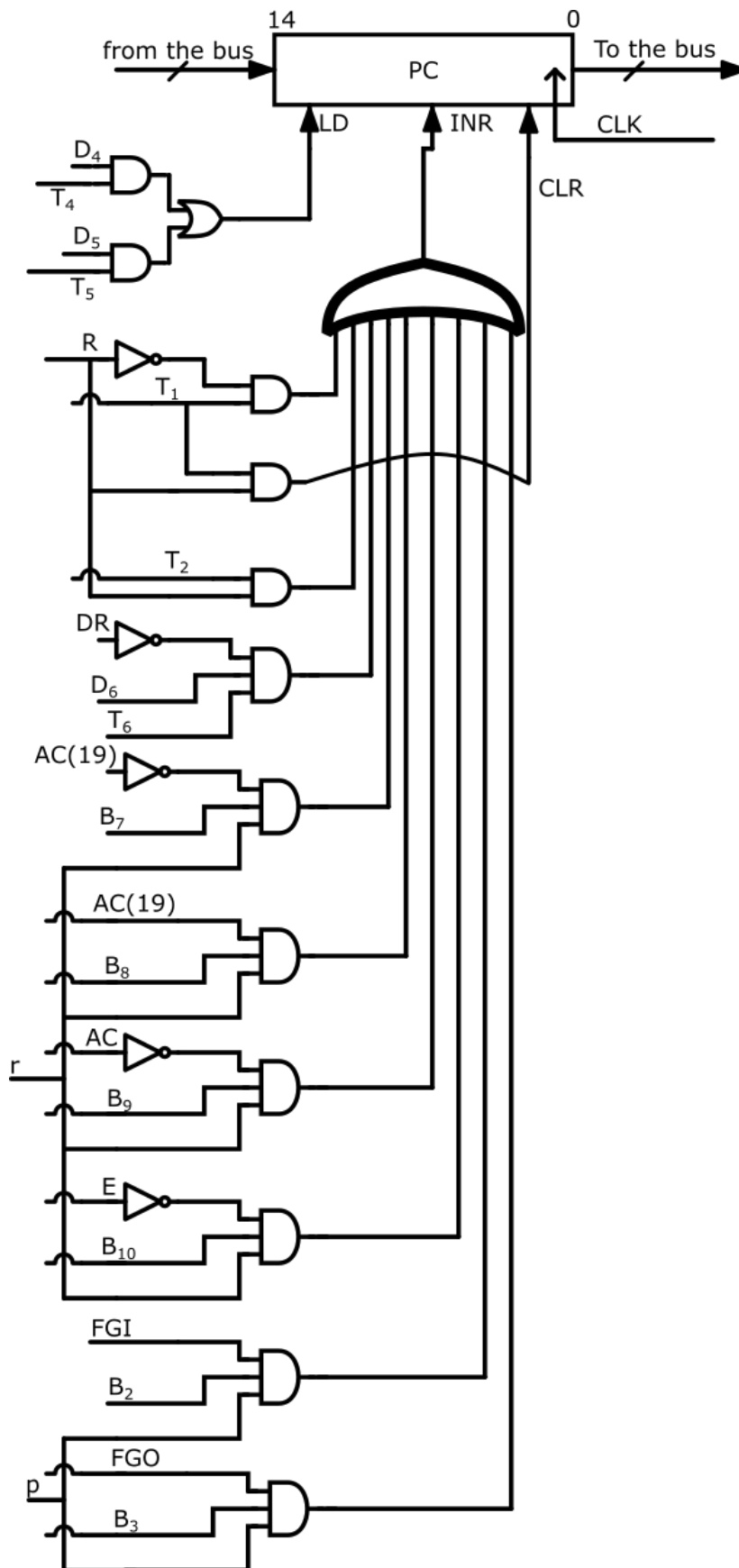


Figure 6: Program Counter

Address Register (AR): Address register is used to hold address stored in IR. We use only AR bits to access memory from memory unit.

Logic for AR can be obtained by OR-ing below conditions.

LD

$R'T_0 : AR \leftarrow PC$

$D_{15}'IT_3 : AR \leftarrow M[AR]$

$R'T_2 : I \leftarrow IR[19], D_0 \dots D_{15} \leftarrow IR[18,17,16,15], AR \leftarrow IR[14-0]$

CLR

$RT_0 : AR \leftarrow 0, TR \leftarrow PC$

INR

$D_5.T_4 : M[AR] \leftarrow PC, AR \leftarrow AR+1$

 


Figure 7: Address Register

Instruction Register (IR): Much about IR has already been discussed above. Its logic can be obtained by OR-ing below conditions.

LD

$R'T_1 : IR \leftarrow M[AR], PC \leftarrow PC+1$

The first bit of IR is used as an I bit and bit 18-15 are decoded using 4*16 decoder as shown in figure below along with design of decoder for RRI and IOI:

Designing decoder for RRI and IOI:

Similar to MRI instruction decoder RRI and IOI also needs decoding. D_{15} decoder output and I bit can identify RRI and IOI but further instruction needs to be decoded from the address bits i.e. 15 bits. But we don't have to decode all 15 bits because we only have total of 20 RRI and IOI altogether so we decode the changing bits.

Let's take a closer look at our bits layout in IR

0 1 1 1 1 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0
 7 8 0 0 0

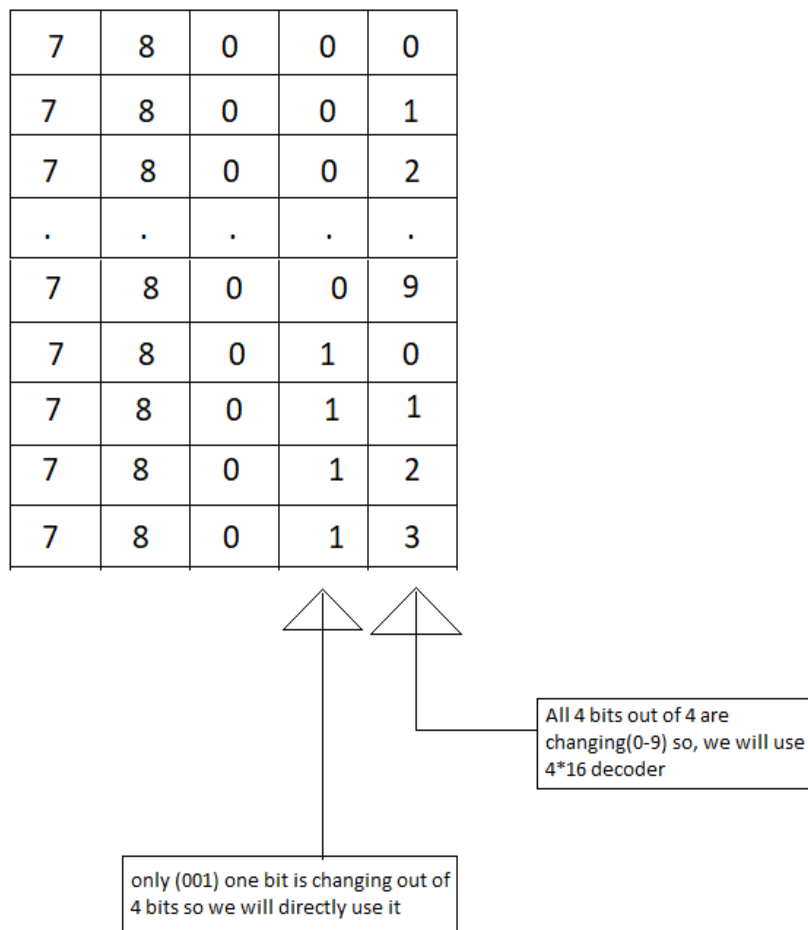


Figure 8: Bit layout in IR

4*16 decoder gives us 10 RRI instructions when D_{15} is active i.e. $B_0 \leftarrow B_9$. As for remaining RRI we AND 5th bit with decoder output to get B_{10} , B_{11} , B_{12} , B_{13} . When D_{15} and I both are active same decoder output $B_0 - B_5$ gives 6 IOI instructions.

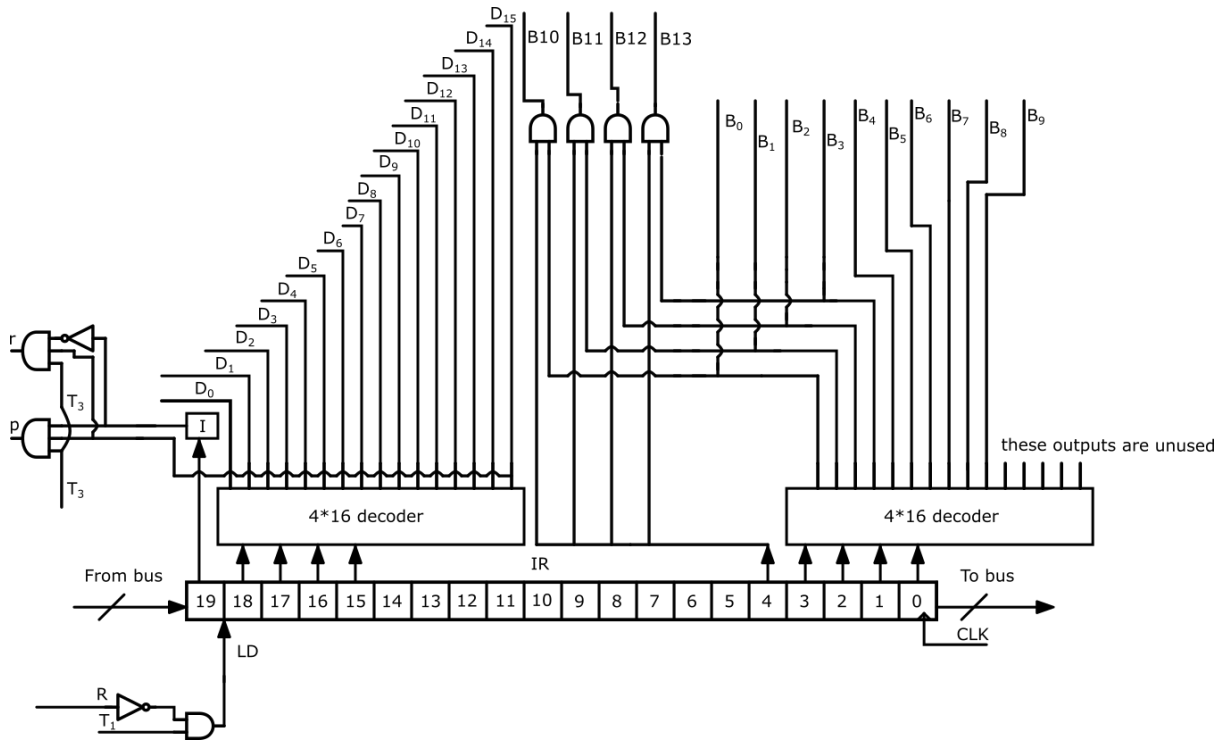


Figure 9: Instruction Register with Decoders

Data Register (DR): Data register holds data stored in memory identified by AR bits. Logic for DR can be obtained by OR-ing below conditions.

LD

$D_6T_4 : DR \leftarrow M[AR]$

$D_0.T_4 : DR \leftarrow M[AR]$

$D_1T_4 : DR \leftarrow M[AR]$

$D_2.T_4 : DR \leftarrow M[AR]$

$D_7T_4 : DR \leftarrow M[AR]$

$D_8T_4 : DR \leftarrow M[AR]$

$D_9T_4 : DR \leftarrow M[AR]$

$D_{10}T_4 : DR \leftarrow M[AR]$

INR

$D_6T_5 : DR \leftarrow DR+1$

 


Figure 10: Data Register

Temporary register (TR): Temporary register like the name says is used for temporarily holding data.

LD

$RT_0 : AR \leftarrow 0, TR \leftarrow PC$

 


Figure 11: Temporary Register

OUTR: Output register holds data loaded by AC onto the bus for output.

LD:

pB₁: OUTR \leftarrow AC (0-9), FGO \leftarrow 0

 


Figure 12: Output Register

INPR: Input register holds data input from the user. It only loads data directly into AC.

 


Figure 13: Input Register

Memory: Much about memory has already been discussed above. Unlike other registers memory is a stack of register. It has 2 input instructions i.e. Read and Write. Based on these instructions it either downloads or uploads a data from or to the bus.

Memory read:

R'T₁ : IR \leftarrow M [AR], PC \leftarrow PC+1

D₀.T₄ : DR \leftarrow M [AR]

D₁T₄ : DR \leftarrow M [AR]

D₂.T₄ : DR \leftarrow M [AR]

D₆T₄ : DR \leftarrow M [AR]

D₇T₄ : DR \leftarrow M [AR]

D₈T₄ : DR \leftarrow M [AR]

D₉T₄ : DR \leftarrow M [AR]

$$D_{15}'IT_3:AR \leftarrow M [AR]$$

Memory write:

 
$$D_3.T_4: M[AR] \leftarrow AC, SC \leftarrow 0$$
$$\text{D}_5.\text{T}_4 : \text{M}[\text{AR}] \leftarrow \text{PC}, \text{AR} \leftarrow \text{AR} + 1$$
$$D_6T_6 : M[AR] \leftarrow DR, \text{ if } (DR=0) \text{ then } (PC \leftarrow PC+1), SC \leftarrow 0$$
$$\text{RT}_1 : \text{M}[\text{AR}] \leftarrow \text{TR}, \text{PC} \leftarrow 0$$


Figure : Memory

E-flip flop:

Design for E- flip flop is slightly more complicated than other flip flops. This is because it is used for storing data and not instructions or flags. But first let's take a look at all instructions storing data in E-flip flop.

$$D_1T_5 : E \leftarrow C_{out}$$
$$D_8T_8: E \leftarrow C_{out}$$
$$\text{rB}_5 : \text{E} \leftarrow \text{AC}(19)$$
$$\text{rB}_3 : E \leftarrow E'$$
$$\text{rB}_4 : E \leftarrow \text{AC}(0)$$
$$\text{rB}_1 : E \leftarrow 0$$

Normally only rB_1 would be connected to k and all the other would be connected to J as shown in the figure below:

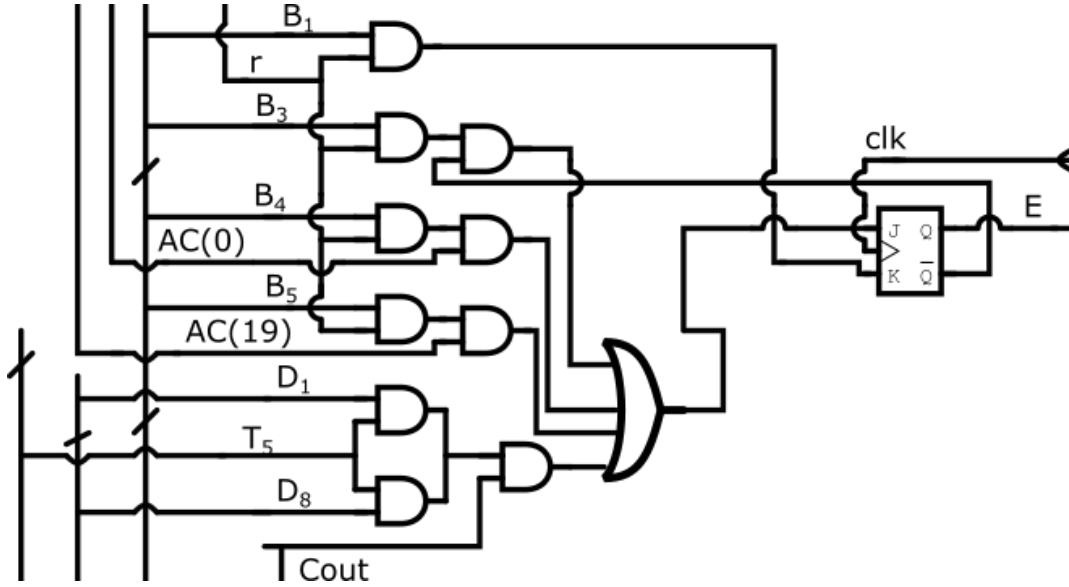


Figure : Wrong Implementation of Flip Flop

But this wouldn't work because C_{out} , $AC(0)$, $AC(19)$ and E' all can have 0 values. Since all instructions are mutually exclusive for $rB_1 = 0$ and any other of above instructions are true then for C_{out} , AC or $E' = 0$, $J = 0$ and $k = 0$.

Eg. for $rB_1 = 0$, $rB_5 = 1$ and $AC(19) = 0$.

In this case we won't be able to store zero value into E-flip flop instead the flip flop retains previous value because $k = 0$ and J also remains 0 since $AC(19)$ is currently 0.

To solve this problem, we came up with a new Boolean expression. Let's make a solution for D_1T_5 and C_{out} as for all other expression we can mimic the same solution.

| D_1T_5 | C_{out} | J | K |
|----------|-----------|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Table 5: J and K for E flip flop

From above table we can see that for $D_1T_5 = 1$ if $C_{out} = 0$ we set k as 1 storing zero value and if $D_1T_5 = 1$ and $c_{out} = 1$ we set $J = 1$ storing 1 value of C_{out} .

We can deduce from above table,

$$J = D_1 \cdot T_5 \cdot C_{out}, \quad k = D_1 \cdot T_5 \cdot C_{out}'$$

Similarly,

$$J = D_8 T_5 C_{out}, k = D_8 T_5 C_{out}'$$

$$J = rB_5.AC(19), k = rB_5.AC(19)'$$

$$J = rB_4.AC(0), k = rB_4.AC(0)'$$

$$J = rB_3.E, k = rB_3.E'$$

As for:

rB_1 : $J=0, k = rB_1$ which sets flip flop as 0.

Hence, the final logic can be obtained by OR-ing all J's and all k's as shown in the figure below:

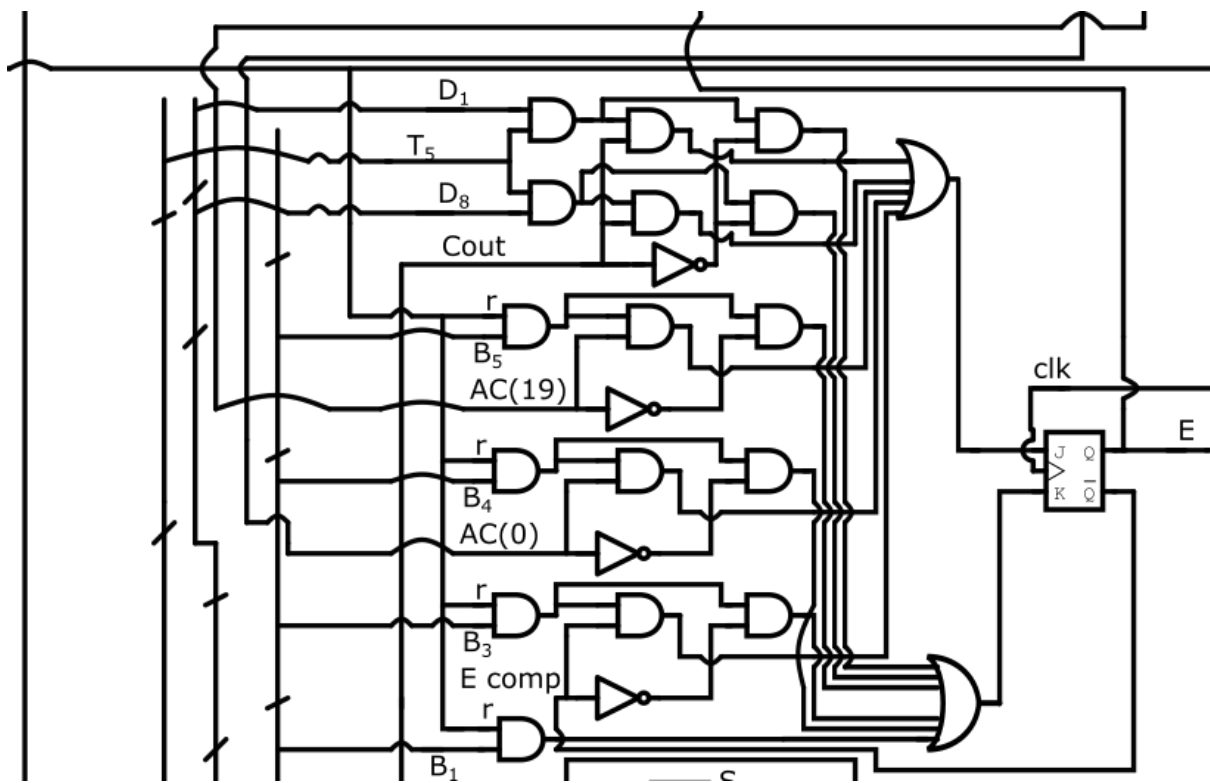


Figure 14: Right Implementation of E flip flop

Start-Stop flip-flop: It is a JK flip-flop that only resets for RB_{11} else it stays 1.

 


Figure 15: Start-stop flip flop

FGI flip flop: It is a JK flip flop that is set to one on input and it retains its value until $PB_0=1$ and the flip flop is reset.

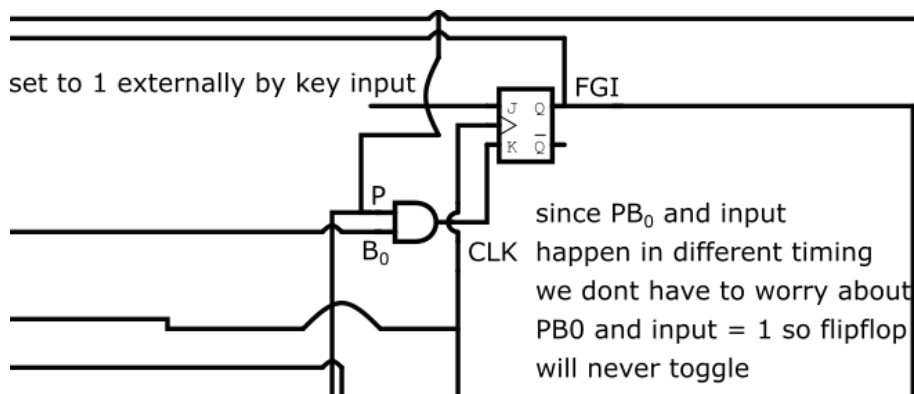


Figure 16: FGI Flip flop

FGO flip flop: It is a JK flip flop that is set to one on output request and it will retain it's value until $PB_1=1$.

 


Figure 17: FGO Flip flop

IEN flip flop: Interrupt enable flag is stored in a JK flip flop whose expressions are listed below:

$RT_2: IEN \leftarrow 0$

$PB_4: IEN \leftarrow 1$

$PB_5: IEN \leftarrow 0$

$K = PB_5 + RT_2$

 


Figure 18: IEN Flip flop

R flip flop: It is a JK flip flop that sets to 1 whenever:

$IEN(FGI + FGO) \cdot T_0' \cdot T_1' \cdot T_2': R \leftarrow 1$

And resets when,

$RT_2: R \leftarrow 0$

 


Figure 19: R Flip flop

Common Bus System (CBS): Peer to Peer connection among registers is too complex and requires too many connection lines so, we use a common bus to connect all these registers or at least those that need the bus. INPR and OUTR does not load anything to the bus, so aside of these two registers, we constructed a CBS that selects one of 7 registers i.e AR, PC, DR, AC, IR, TR and M[AR] (here M[AR] refers to one register from the stack of registers in the memory identified by the address stored in AR).

We used 8*1 MUX to select one of the 7 registers inputs and use one extra input for null value i.e empty input (no register selected) as shown below in the figure. Since, we have max 20 bit registers we will need 20 MUX from 8*1 MUX (0) to 8*1 MUX (19), along with three selection lines to choose one of 8 inputs among all MUX. 20 MUX all together will contribute to 20 bit CBS.

For MUX 15 to MUX 19 we have set AR and PC inputs to 0 since they only have 15 bits.

| Input for 8*3 encoder | | | | | | | Selection Lines for MUX | | | Register |
|-----------------------|----------------|----------------|----------------|----------------|----------------|----------------|-------------------------|----------------|----------------|----------|
| X ₁ | X ₂ | X ₃ | X ₄ | X ₅ | X ₆ | X ₇ | S ₂ | S ₁ | S ₀ | |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | None |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | AR |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | PC |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | DR |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | AC |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | IR |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | TR |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | Memory |

Table 6: Encoder to selection line

$$S_0 = x_1 + x_3 + x_5 + x_7$$

$$S_1 = x_2 + x_3 + x_6 + x_7$$

$$S_2 = x_4 + x_5 + x_6 + x_7$$

Each input for the encoder selects a unique register to be loaded in the bus. We only load the data to the bus however downloading it into registers is done by the register load or LD logic. So, while constructing “select” logic for a register we only considered micro-operation involving that register as the source like $PC \leftarrow AR$ etc. and the destination being another register through the bus like $DR \leftarrow M[AR]$.

In some cases, like in $AC \leftarrow DR$ bus is not involved in fact AC does not receive any data from the bus, it only receives data from either ALU or E Flip flop and only loads the data to the bus. So, any operation involving AC as a destination is not considered.

OUTR Register only downloads the data from the bus and doesn't load anything to it so it's not considered. INPR is not connected to the bus at all so it is also not considered so we are only concerned with 6 registers and 1 memory unit.

Logic for x_1 i.e, AR

$$D_4T_4 : PC \leftarrow AR$$

$$D_5T_5 : PC \leftarrow AR$$

Logic for x_2 i.e, PC

$$R'T_0 : AR \leftarrow PC$$

$$D_5T_4 : M[AR] \leftarrow PC$$

Logic for x_3 i.e, DR

$$D_6T_6 : M[AR] \leftarrow DR$$

Logic for x_4 i.e, AC

$$D_3T_4 : M[AR] \leftarrow AC$$

$$PB_1 : OUTR \leftarrow AC(0-9)$$

Logic for x_5 i.e, IR

$$R'T_2 : AR \leftarrow IR(14-0)$$

Logic for x_6 i.e, TR

$RT_1 : M[AR] \leftarrow TR$

Logic for x_7 i.e Memory

$R'T_1 : IR \leftarrow M[AR], PC \leftarrow PC+1$

$D_0.T_4 : DR \leftarrow M[AR]$

$D_1.T_4 : DR \leftarrow M[AR]$

$D_2.T_4 : DR \leftarrow M[AR]$

$D_6.T_4 : DR \leftarrow M[AR]$

$D_7.T_4 : DR \leftarrow M[AR]$

$D_8.T_4 : DR \leftarrow M[AR]$

$D_9.T_4 : DR \leftarrow M[AR]$

$D_{10}.T_4 : DR \leftarrow M[AR]$

$D_{15}.IT_3 : AR \leftarrow M[AR]$

 


Figure 20: Common Bus System

ALU (Arithmetic Logic Shift Unit):

ADD and Subtraction: These two operations are performed by a single unit consisting of 2*1 MUX 1 inverter two AND gates and a single full adder. In this way not only can we simplify two operations but also make individual ALU units compact.

 


Figure 21: Add and subtract logic

Addition: For addition we will pass '0' as selection signal for MUX selecting AC(i) and DR(i) which will be added by a full adder under C_{in} 0 and releases a C_{out} which will be later stored in E flip flop. Under the control signal AND it will be passed into AC.

$$AC(i) + DR(i) + C_{in}(0) = \text{result} + C_{out}$$

$$E \leftarrow C_{out}$$

$$AC(i) \leftarrow \text{result}$$

Subtraction: A subtraction using 2's complement is $AC(i) + DR(i)' + 1$

Hence, MUX selection signal becomes one. For C_{in} 1 will be passed.

$$AC(i) + DR(i)' + C_{in}(1) = \text{Result} + C_{out}$$

$$E \leftarrow C_{out}$$

$$AC(i) \leftarrow \text{result}$$

NAND: Performed using two inverters, one OR gate and the result is passed through AC when NAND control signal is 1.

$$AC(i)' + DR(i)'$$

DR or LDA: Under signal DR, DR(i) is loaded to the AC

$$AC(i) \leftarrow DR(i)$$

XOR: Under signal XOR

$$AC(i) \leftarrow AC(i) \oplus DR(i)$$

COMP: When COMP = 1

$$AC(i) \leftarrow AC(i)'$$

IR: When IR=1

$$AC(i) \leftarrow IR(i)$$

DRCOMP: When DRCOMP = 1

$$AC(i) \leftarrow DR(i)'$$

INPR: When INPR = 1

$$AC(i) \leftarrow INPR(i)$$

Since INPR is only 10 bits it will fill up AC(0-9) using ALU units (0-9), all other bits will be zero because ALU units (10-19) will stay low.

SHR: When $\text{SHR} = 1$

$$\text{AC}(i) \leftarrow \text{AC}(i + 1)$$

i.e, for $\text{AC}(18) \leftarrow \text{AC}(19)$

But if $i = 19$ then $i + 1 = 20$, 20th bit doesn't exist so the signal for $\text{AC}(i + 1)$ will remain low hence ALU will store 0 in 19th bit but immediately E flip flop will store its value in 19th bit in the same clock cycle making it a circular right shift.

SHL: For $\text{SHL} = 1$

$$\text{AC}(i) \leftarrow \text{AC}(i - 1)$$

i.e, for $\text{AC}(17) \leftarrow \text{AC}(16)$

If $i = 0$ then $\text{AC}(i - 1) = \text{AC}(-1)$ which does not exist so $\text{AC}(i - 1)$ signal will stay low and ALU will store 0 in 0th bit. But immediately E flip flop will store its value in 0th bit in the same clock cycle making it a circular left shift.

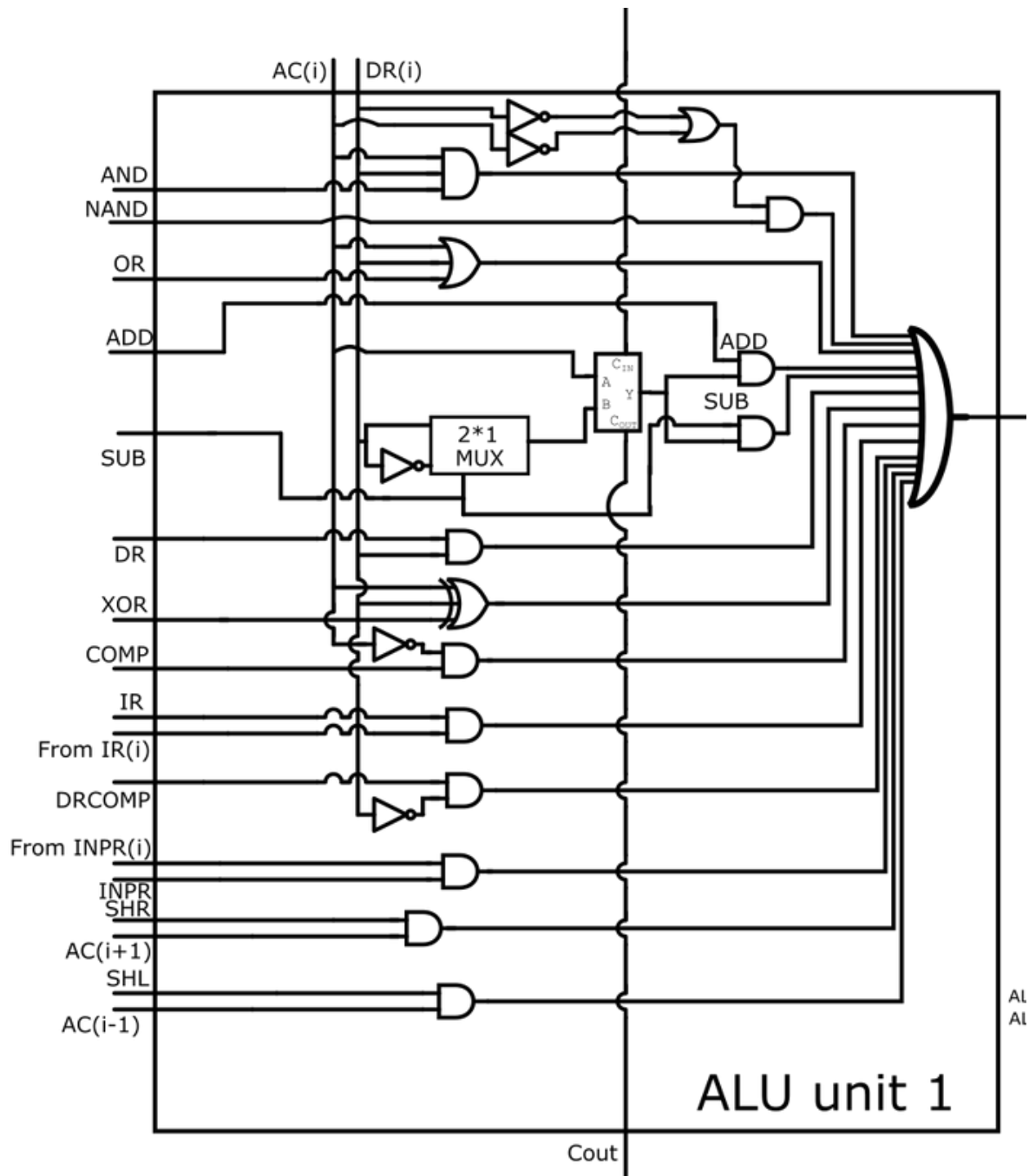


Figure 22: Single stage ALU

AC(ACCUMULATOR): It's a 20-bit register used for temporarily storing intermediate arithmetic and logical operation values. Unlike most other registers it doesn't receive any values from CBS, it only loads values to the CBS. Any value stored in AC comes from ALU. List of LD, INR and CLR logic for AC are listed below.

LD:

D₀.T₅ : $AC \leftarrow AC \text{ AND } DR$, $SC \leftarrow 0$

D₁T₅ : $AC \leftarrow AC + DR$, $E \leftarrow C_{out}$, $SC \leftarrow 0$

D₂.T₅ : AC←DR, SC←0

D₇T₅ : AC←AC v DR, SC←0

D₈T₅ : AC←AC - DR, E_S←C_{out}, SC←0

D₉T₅ : AC←AC⊕DR, SC←0

D₁₀T₅ : AC←AC NAND DR, SC←0

rB₂ : AC←AC

rB₄ : AC←shr (AC), AC(19)←E, E←AC(0)

rB₅ : AC←shl (AC), AC(0)←E, E←AC(19)

PB₀ : AC(0-9)←INPR, FGI←0

rB₁₂ : AC←IR

rB₁₃ : AC←DR

CLR:

rB₀ : AC←0

INR:

rB₆ : AC←AC+1

These control signals are also shared by the ALU for its operations.

In addition to these signals AC (9) and AC (19) also receives bits from E flip flop when SHL and SHR signals are active.

AC (19) ←E.SHR

AC (0) ←E.SHL

For SHR or SHL =1, AC receives whatever is stored in E flipflop.

